

Andy's HSH wiring scheme:

Toggles between SSS and HH configuration

Notes:

1) I found fitting the 4PDT switch to be quite a squeeze in between the two pots on my guitar, this layout diagram is deliberately more spacious for the sake of clarity!

2) I've implemented a star-grounding scheme to avoid ground loops (see www.guitarnuts.com/wiring/shielding/shield3.php) which is shown here. The guitar's control cavity is also fully shielded with copper foil and there is a connection from the ground point (the washer) to the shield.

3) I've used some shielded wire to the output on my guitar, which isn't shown here to simplify the diagram

3) Pickup wiring colours are the Seymour Duncan colour scheme

